

BBM233: Logic Design Lab
2021 Fall
Lab Experiment #2 Report

Mert Ali Yalçın 21946682

October 29, 2021

Question 1

- What does a universal gate mean?

A universal gate is a gate which can implement any Boolean function without need to use any other gate type.

- Which logic gates are universal gates?

NAND and NOR gates are universal gates.

Question 2

Implementing other logic gates by using only the universal gates: 1 2

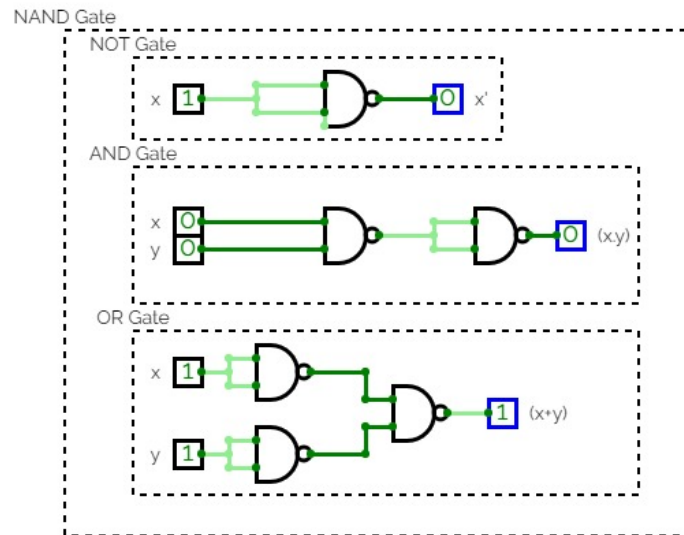


Figure 1: Implementing other gates using only NAND gate

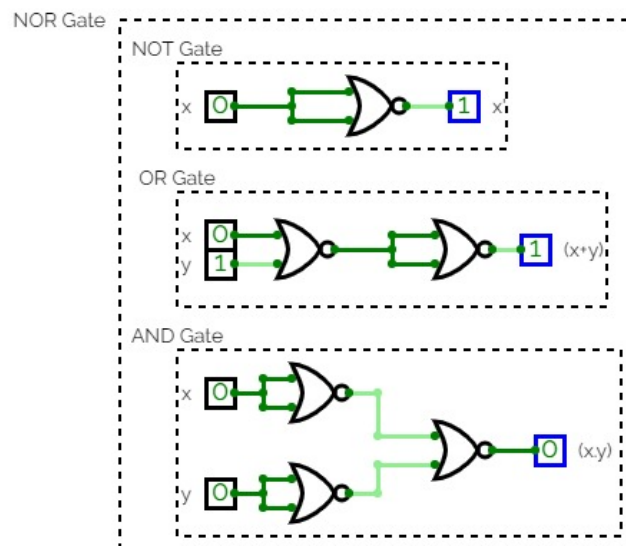


Figure 2: Implementing other gates using only NOR gate

Question 3

A Boolean function is given: $F(A, B, C, D) = \sum(0, 2, 8, 10, 11)$

- Simplify F using a Karnaugh Map to obtain a Boolean function in sum-of-products form, 1

AB\CD	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	1	1

Table 1: Simplifying the the F(A,B,C,D)

$$F(A, B, C, D) = B'D' + AB'C$$

Since the question asks us to show the equation F(A,B,C,D) in "sum-of-products" form, we should multiply our terms accordingly:

$$F(A, B, C, D) = B'D'(A + A')(C + C') + AB'C(D + D')$$

Resulting;

$$F(A, B, C, D) = A'B'C'D' + A'B'CD' + AB'C'D' + AB'CD' + AB'CD$$

- Use the formula you obtained from the K-Map and express it using only NAND gates. You may find using De Morgan's Laws useful,

$$F(A, B, C, D) = B'D' + AB'C = ((B'D')'.(AB'C)')'$$

- Do the same but this time using only NOR gates.

$$F(A, B, C, D) = B'D' + AB'C = (((B + D)' + (A' + B + C')')')'$$

References

- BBM231 Lecture Notes
- <http://www.uop.edu.pk/ocontents/Lec-10-universal%20gates.pdf>